

85%

HW2A Modern Control Theory


Master of Science in Electrical Engineering

Davalos Gonzalez Erick Christopher

Problem 1)

(25 %) Find the (a) loop, (b) node, and (c) state equations for the circuit shown in Figure. For points (a) and (b) write the matrix integro-differential equations, respectability.

20%

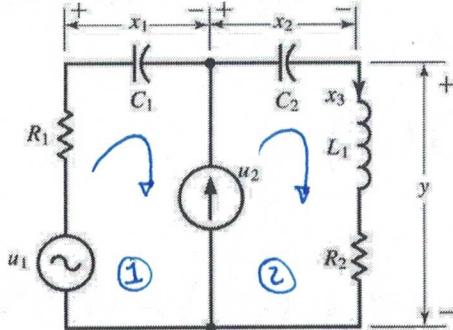

a) $\sum V = 0$


$$\checkmark \quad i_1(t) = i_2(t) - v_2(t)$$

① $i_2(t) - i_1(t) = v_2(t)$

$$i_2(t) = v_2(t) + i_1(t)$$

② Using the supernode
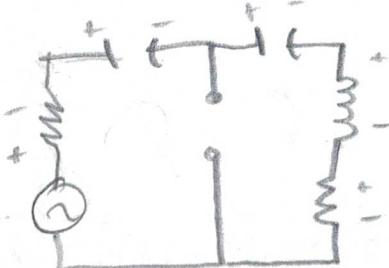
$$V_{R1} + V_{C1} + V_{C2} + V_{L1} + V_{R2} = u_1(t)$$



$$R_1 i_1(t) + \frac{1}{C_1} \int i_1(t) dt + \frac{1}{C_2} \int i_2(t) dt + L \frac{di_2(t)}{dt} + R_2 i_2(t) = u_1(t)$$

Dividing both sides $\left(\frac{d}{dt}\right)$

$$R_1 \frac{di_1(t)}{dt} + \frac{i_1(t)}{C_1} + \frac{i_2(t)}{C_2} + L \frac{d^2 i_2(t)}{dt^2} + R_2 \frac{di_2(t)}{dt} = \frac{d u_1(t)}{dt}$$

Let $\frac{df(t)}{dt} = D(f)$, using $x_2(t) = v_2(t) + i_1(t)$

* Grouping for i_1

$$R_1 \cdot D(i_1) + \frac{i_1(t)}{C_1} + \frac{v_2(t)}{C_2} + \frac{i_1(t)}{C_2} + L^2(v_2 + i_1) + \dots =$$

$$+ R_2 \cdot D(v_2 + i_1) = D(v_1)$$

$$i_1(t) \cdot (R_1 \cdot D + \frac{1}{C_1} + \frac{1}{C_2} + LD^2 + R_2 D) = v_1(t) \cdot D - \dots$$


$$- v_2(t) \left(\frac{1}{C_2} + LD^2 + R_2 D \right)$$

Matrix form of a)

$$\begin{matrix} 5 \times 1 \\ \begin{bmatrix} R_1 D \\ \frac{1}{C_1} \\ \frac{1}{C_2} \\ LD^2 \\ R_2 D \end{bmatrix} \end{matrix} \begin{matrix} 1 \times 1 \\ [i_1(t)] \end{matrix} = \begin{matrix} [v_1(t)] \\ [D] \end{matrix} - \begin{matrix} 5 \times 1 \\ \begin{bmatrix} 0 \\ 0 \\ \frac{1}{C_2} \\ LD^2 \\ R_2 D \end{bmatrix} \end{matrix} \begin{matrix} 1 \times 1 \\ [v_2(t)] \end{matrix}$$

Esta operación no es correcta.

⑤ Nodes

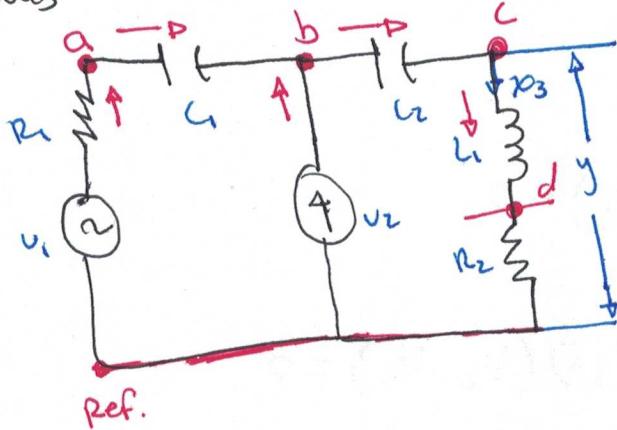

$$\sum_{n=1}^N i_n = 0.$$

$$④ \underline{i_{a1} - i_{c1} = 0} \rightarrow \frac{v_a - v_1(t)}{R_1} - C_1 \frac{d(v_a - v_b)}{dt} = 0$$

$$⑤ \underline{i_{c1} + v_2(t) - i_{c2} = 0} \rightarrow C_1 \frac{d(v_b - v_a)}{dt} + v_2(t) - C_2 \frac{d(v_b - v_c)}{dt} = 0$$

$$⑥ \underline{i_{c2} - i_{d1} = 0} \rightarrow C_2 \frac{d(v_c - v_b)}{dt} - \frac{1}{L_1} \int (v_c - v_d) dt = 0$$

$$⑦ \underline{i_{d1} - i_{d2} = 0} \rightarrow \frac{1}{L_1} \int (v_d - v_c) dt - \frac{v_d}{R_2} = 0 \quad \checkmark$$

*Dening ⑥ and ⑦ to have only differential functions


$$⑧ \underline{C_1 \frac{d^2(v_c - v_b)}{dt^2} - \frac{1}{L_1} (v_c - v_d) = 0}$$

$$⑨ \underline{\frac{1}{L_1} (v_d - v_c) - \frac{d(v_d)}{dt} \cdot \frac{1}{R_2} = 0} \quad \checkmark$$

⑩

Pase ③

Let $\frac{d(f(t))}{dt} = D(f)$

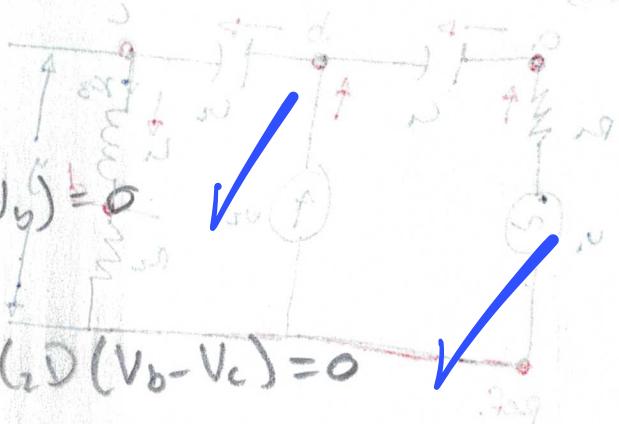

$$\textcircled{a} \quad \frac{V_a - V_1(t)}{R_1} - C_1 D(V_a - V_b) = 0$$

$$\textcircled{b} \quad C_1 \cdot D(V_b - V_a) + V_2(t) - C_2 D(V_b - V_c) = 0$$

$$\textcircled{c} \quad C_2 D^2 (V_c - V_b) - \frac{1}{L_1} (V_c - V_d) = 0$$

$$\textcircled{d} \quad \frac{1}{L_1} (V_d - V_c) - \frac{D(V_d)}{R_2} = 0$$

Grouping similar terms

$$\textcircled{a} \quad V_a \left(\frac{1}{R_1} - C_1 D \right) + V_b (C_1 \cdot D) = \frac{U_1(t)}{R_1}$$

$$\textcircled{b} \quad V_a (-C_1 D) + V_b (C_1 D - C_2 D) + V_c (C_2 D) = -U_2(t)$$


$$\textcircled{c} \quad V_b (-C_2 D^2) + V_c (C_2 D^2 - \frac{1}{L_1}) + V_d (\frac{1}{L_1}) = 0$$

$$\textcircled{d} \quad V_c (\frac{1}{L_1}) + V_d (\frac{1}{L_1} - \frac{D}{R_2}) = 0$$

In the next page the matrix form is shown.

Matrix form of b)
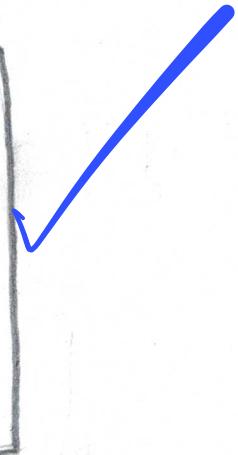
$$\begin{bmatrix} \frac{1}{R_1} - C_1 D & C_1 D & 0 & 0 \\ -C_1 D & C_1 D - C_2 D & C_2 & 0 \\ 0 & -C_2 D^2 & C_2 D - \frac{1}{L_1} & \frac{1}{L_1} \\ 0 & 0 & -\frac{1}{L_1} & \frac{1}{L_1} - \frac{D}{R_2} \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix} = \begin{bmatrix} \frac{V_a(t)}{R_1} \\ -V_b(t) \\ 0 \\ 0 \end{bmatrix}$$



c) State equations.

Solving with KVL (Mesh analysis)

Using the loop equations in a) let $x_1 = V_{c1}$

$x_2 = V_{c2}$, $x_3 = i_{L1}$

$$① \underline{x_3 - \underline{i}_1(t)} = \underline{v_2(t)} \longrightarrow \underline{i_1(t)} = \underline{x_3 - v_2(t)}$$

$$② V_{R1} + V_{c1} + V_{c2} + V_{L1} + V_{R2} = V_1(t)$$

$$R_1(x_3 - v_2(t)) + x_1 + x_2 + L\dot{x}_3 + R_2x_3 = V_1(t)$$

$$L\dot{x}_3 + x_3(R_1 + R_2) + x_1 + x_2 - R_1v_2(t) = V_1(t)$$

$$\dot{x}_3 = \frac{1}{L}V_1(t) + \frac{R_1}{L}v_2(t) - \frac{1}{L}x_1 - \frac{1}{L}x_2 - x_3 \left(\frac{R_1 + R_2}{L} \right)$$

In page 3 from node equations (b) and (c)

$$(b) i_{C1} + v_2(t) - i_{C2} = 0$$

$$(c) i_{C2} - i_{L1} = 0$$

From (b)

$$C_1 \dot{v}_1 + v_2(t) - C_2 \dot{v}_2 = 0$$

$$\dot{x}_1 = \frac{C_2 \dot{v}_2 - v_2(t)}{C_1} = \frac{C_2}{C_1} \dot{v}_2 - \frac{v_2(t)}{C_1} \quad (1)$$

From (c)

$$C_2 \frac{dv_{C2}}{dt} = i_{L1} \rightarrow C_2 \dot{v}_2 = x_3 \rightarrow \dot{v}_2 = \frac{x_3}{C_2} \quad (2)$$

Using (1) and (2)

$$\dot{x}_1 = \frac{C_2}{C_1} \left(\frac{x_3}{C_2} \right) - \frac{v_2(t)}{C_1} = \frac{x_3}{C_1} - \frac{v_2(t)}{C_1}$$

$$\dot{x} = Ax + Bu$$

$$\begin{bmatrix} \dot{i}_{C1} \\ \dot{i}_{C2} \\ \dot{v}_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 & \frac{1}{C_1} \\ 0 & 0 & \frac{1}{C_2} \\ -\frac{1}{L} & -\frac{1}{L} & -\frac{(R_1+R_2)}{L} \end{bmatrix} \begin{bmatrix} v_{C1} \\ v_{C2} \\ i_L \end{bmatrix} + \begin{bmatrix} 0 & -\frac{1}{C_1} \\ 0 & 0 \\ \frac{R_1}{L_1} \end{bmatrix} \begin{bmatrix} u_1(t) \\ u_2(t) \end{bmatrix}$$

$$y = V_{L1} + V_{R2} = L \frac{d i_2(t)}{dt} + x_1(t) \cdot R_2$$

$$y = L \ddot{x}_3 + x_3 \cdot R_2$$

$$y = k \left(\frac{1}{L} v_1(t) + \frac{R_1}{L} v_2(t) - \frac{1}{k} x_1 - \frac{1}{k} x_2 - x_3 \left(\frac{R_1 + R_2}{k} \right) \right) + x_3 \cdot R_2$$


$$y = v_1(t) + R_1 v_2(t) - x_1 - x_2 - x_3 \cdot R_1$$

$$y = Gx + Du$$

$$y = \begin{bmatrix} 1 & -1 & -R_1 \end{bmatrix} \begin{bmatrix} 3 \times 1 \\ v_{C1} \\ v_{C2} \\ i_L \end{bmatrix} + \begin{bmatrix} 1 & R_1 \end{bmatrix} \begin{bmatrix} 2 \times 1 \\ v_1(t) \\ v_2(t) \end{bmatrix}$$


(25 %) Write the state equations for the following linear time-invariant networks in Fig.2, assuming that all the R 's, C 's, and L 's are time-invariant, and (a) using charges and fluxes as state variables and (b) using capacitor voltage and inductor currents as the state variables.

Wahl
Problem 2

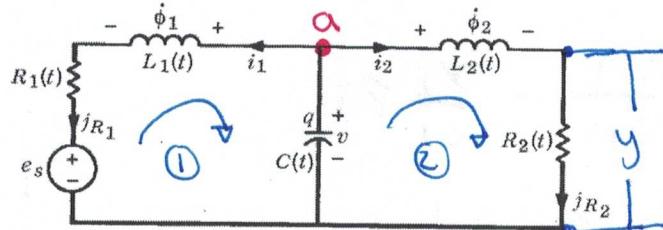

a) Using KVL we set an arbitrary current for each loop.

$$\textcircled{1} \quad V_{R1} + V_{L1} + V_{C1} = V_{es} \quad \left\{ \begin{array}{l} Q_C = x_1 = C \cdot V(t) \\ \phi_{L1} = x_2 = L_1 i_1(t) \end{array} \right. \quad \checkmark$$

$$\textcircled{2} \quad V_{L2} + V_{R2} - V_{C1} = 0 \quad \left\{ \begin{array}{l} \phi_{L2} = x_3 = L_2 i_2(t) \\ V_L = L \frac{di}{dt} \end{array} \right. \quad \checkmark$$

$$\frac{x_2}{L_1} = i_1(t); \frac{x_3}{L_2} = i_2(t) \quad \left\{ \begin{array}{l} i_1 = C \frac{dv}{dt} \\ i_2 = \frac{d\phi_{L2}}{dt} \end{array} \right. \quad \checkmark$$

$$\left(\frac{\dot{x}_2}{L_1} = \frac{di}{dt} \right) \cdot L_1 = \dot{x}_2 = \frac{L_1 di}{dt} = \dot{V}_{L1} \quad \sim$$

$$\textcircled{1} \quad \frac{x_2}{L_1} \cdot R_1 + \dot{x}_2 + \frac{x_1}{C_1} = V_{es}$$

$$\textcircled{2} \quad \dot{x}_3 + \frac{x_3}{L_2} \cdot R_2 - \frac{x_1}{C_1} = 0$$

Analyzing node a we have $i_{L1} + i_{L2} + i_C = 0$

$$\dot{i}_C = -i_{L1} - i_{L2}; \quad i_C = \frac{dQ_C}{dt}$$

$$\left[\dot{x}_1 = -\frac{x_2}{L_1} - \frac{x_3}{L_2} \right] \quad \textcircled{3}$$

From ①, ② and ③

①

$$\dot{x}_2 = V_{CS} - \frac{x_1}{C_1} - \frac{x_2}{L_1} \cdot R_1$$

Simplifying

$$② \dot{x}_3 = \frac{x_1}{C_1} - \frac{x_3}{L_2} \cdot R_2$$

③

$$\dot{x}_1 = -\frac{x_2}{L_1} - \frac{x_3}{L_2}$$

$$\begin{bmatrix} \dot{q} \\ \dot{\phi}_1 \\ \dot{\phi}_2 \end{bmatrix}$$

$$\dot{x} = Ax + Bu$$

$$\begin{bmatrix} i \\ V_{L1} \\ V_{L2} \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L_1} & -\frac{1}{L_2} \\ \frac{-1}{C_1} & 0 & 0 \\ \frac{1}{C_1} & 0 & -\frac{R_2}{L_2} \end{bmatrix} \begin{bmatrix} Q_C \\ \phi_{L1} \\ \phi_{L2} \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix} [V_{CS}]$$

$$y = (x+Du) : y = V_{R2} = \lambda_2(t) \cdot R_2 = \frac{x_3}{L_2} \cdot R_2 \quad \checkmark$$

$$y = \begin{bmatrix} 0 & 0 & \frac{R_2}{L_2} \end{bmatrix} \begin{bmatrix} Q_C \\ \phi_{L1} \\ \phi_{L2} \end{bmatrix} + \begin{bmatrix} 0 \end{bmatrix} [V_{CS}] \quad \cancel{+}$$

b) Capacitor and inductor currents as state variables.

$$x_1 = V_C = \frac{1}{C_1} \int i_C dt + i_{C0}(t) \quad \dot{x}_1 = \frac{i_C(t)}{C_1}$$

$$x_2 = i_{L1} = \frac{1}{L_1} \int v_{L1} dt + v_{L10}(t) \quad \dot{x}_2 = \frac{v_{L1}(t)}{L_1}$$

$$x_3 = i_{L2} = \frac{1}{L_2} \int v_{L2} dt + v_{L20}(t) \quad \dot{x}_3 = \frac{v_{L2}(t)}{L_2}$$

$\sum V = 0$. From ① and ② of a) in page 8.

$$\textcircled{1} V_{R1} + V_{L1} + V_{C1} = V_{CS} \quad \textcircled{2} V_{L2} + V_{R2} - V_{C1} = 0$$

$$i_1 + i_2 + i_C = 0 \quad \text{Revisur} \downarrow$$

$$\begin{cases} \textcircled{1} \underline{x_2 R_1 + L_1 \dot{x}_2 + x_1 = V_{CS}} & \left\{ \begin{array}{l} i_C(t) = (i_1 - i_2) \\ x_1(t) = (x_2 - x_3) \end{array} \right. \\ \textcircled{2} \underline{L_2 \dot{x}_3 + x_3 \cdot R_2 - x_1 = 0} & \end{cases}$$

$$\dot{x}_1 = -\frac{x_2 - x_3}{C_1} \quad \checkmark$$

$$\dot{x}_2 = \frac{V_{CS}}{L_1} - \frac{x_1}{L_1} - \frac{x_2 R_1}{L_1} \quad \checkmark$$

$$\dot{x}_3 = \frac{x_1}{L_2} - \frac{x_3 R_2}{L_2} \quad \checkmark$$

$$\dot{x} = Ax + Bu$$

etwa 3 Minuten später (durchgezogene Linie)

Revisor

$$\begin{bmatrix} i_{L1} \\ V_{L1} \\ V_{L2} \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L_1} & -\frac{1}{L_1} \\ -\frac{1}{L_1} & \frac{-R_1}{L_1} & 0 \\ \frac{1}{L_2} & 0 & \frac{-R_2}{L_2} \end{bmatrix} \begin{bmatrix} V_{C1} \\ i_{L1} \\ i_{L2} \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$


$$y = V_{R2} = i_2(t) \cdot R_2 = x_3 \cdot R_2 \quad \checkmark$$

$$y = [0 \ 0 \ R_2] \begin{bmatrix} V_{C1} \\ i_{L1} \\ i_{L2} \end{bmatrix} + [0] [V_{Cs}]$$

20%

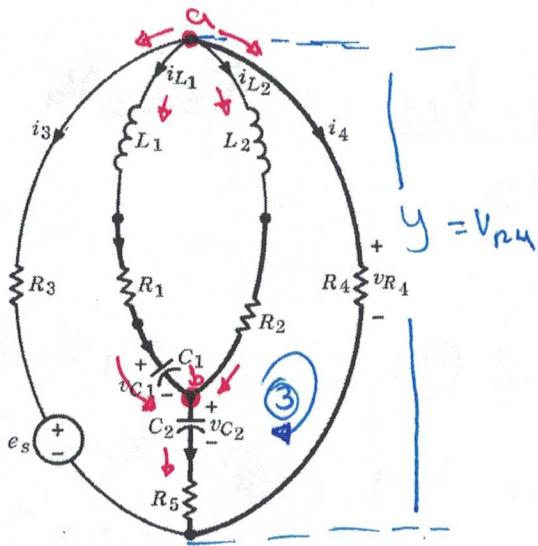Problem 3

(25 %) Write the state equations for the following linear time-invariant networks in Fig.3, assuming that all the R 's, C 's, and L 's are time-invariant and using capacitor voltage and inductor currents as the state variables.



Statement ①

Parallel circuits have the same voltage. The two branches between nodes a and b have the same voltage.

$$\textcircled{1} \quad V_{L1} + V_{R1} + V_{C1} = V_{L2} + V_{R2}$$

Statement ②

Currents flowing in a node is the same as leaving the node.

In node b two currents in one current out.

$$\textcircled{2} \quad i_{C2} = i_{L1} + i_{L2} \quad \textcircled{2.1} \quad i_{R3} + i_{L1} + i_{L2} + i_{R5} = 0$$

Statement ③

The sum of voltage drops along a closed loop is 0.

For loop 3

$$\textcircled{3} \quad V_{R4} + V_{R5} - V_{C2} + V_{R2} + V_{L2} = 0$$

check

Statement ④ The current through a resistor is the voltage difference in its terminals divided by its resistance.

$$④ i_{R3} = \frac{V_{R4} - V_{es}}{R_3}$$

$$\checkmark V_{R4} = V_a$$

~ ~ ~ ~

From ② and ④

$$\dot{i}_{R3} = -\dot{i}_1 - \dot{i}_{L2} - \dot{i}_{R4}$$

$$x_1 = \dot{i}_{L1}(t)$$

$$x_2 = \dot{i}_{L2}(t)$$

$$x_3 = V_{C1}(t)$$

$$x_4 = V_{C2}(t)$$

$$\frac{V_{R4} - V_{es}}{R_3} = -x_1 - x_2 - \frac{V_{R4}}{R_4}$$

$$V_{R4} \left(\frac{1}{R_3} - \frac{1}{R_4} \right) = -x_1 - x_2 + \frac{V_{es}}{R_3}$$

$$V_{R4} = (R_3 - R_4) \left(-x_1 - x_2 - \frac{V_{es}}{R_3} \right) \quad | \quad ⑤$$

Esto no es posible

From ③ and ⑤

$$V_{en} + V_{es} - V_{C2} + V_{C2} + V_{L2} = 0$$

$$(R_3 - R_4) \left(-x_1 - x_2 - \frac{V_{es}}{R_3} \right) + (L_2 \dot{x}_4) R_5 - x_4 + x_2 R_2 + L_2 \ddot{x}_2 = 0 \quad ⑥$$

From ②

$$\dot{i}_{C2} = \dot{i}_{L1} + \dot{i}_{L2}$$

$$L_2 \dot{x}_4 = x_1 + x_2 \rightarrow \dot{x}_4 = \frac{x_1}{C_2} + \frac{x_2}{C_2} \quad | \quad ⑦$$

(5) ~~339~~

Pase ⑬.

Using ⑥ and ⑦ to find \dot{x}_2

$$(R_3 - R_4)(-x_1 - x_2 - \frac{V_{cs}}{R_3}) + L_2 \left(\frac{x_1}{L_2} + \frac{x_2}{L_2} \right) \cdot R_5 - x_4 + x_2 R_2 + L_2 \dot{x}_2 = 0$$

$$L_2 \dot{x}_2 = x_4 - x_1 R_5 - x_2 R_5 - (R_3 - R_4)(-x_1 - x_2 - \frac{V_{cs}}{R_3}) - x_2 R_2$$

$$L_2 \dot{x}_2 = x_4 - x_1 R_5 - x_2 R_5 + (R_3 - R_4)(x_1 + x_2 + \frac{V_{cs}}{R_3}) - x_2 R_2$$

$$\dot{x}_2 = \frac{x_4 + x_1 (R_3 - R_4 - R_5)}{L_2} + \frac{x_2 (R_3 - R_4 - R_5 - R_2)}{L_2} + \frac{V_{cs} (R_3 - R_4)}{L_2 R_3} \quad ⑧$$

We know that currents in series the current of all elements is the same

$$i_{C1} = i_{L1} \rightarrow C_1 \dot{x}_3 = x_1 \rightarrow \dot{x}_3 = \frac{x_1}{C_1} \quad ⑨$$

From equation ①

$$① V_{L1} + V_{m1} + V_{c1} = V_{L2} + V_{m2} \quad ⑩$$

$$L_1 \dot{x}_1 + x_1 \cdot R_1 + x_3 = L_2 \dot{x}_2 + x_2 \cdot R_2$$

Using ⑩ and ⑧ to find \dot{x}_1

$$L_1 \dot{x}_1 + x_1 R_1 + x_3 = x_4 + x_1 (R_3 - R_4 - R_5) + x_2 (R_3 - R_4 - R_5 - R_2) + \frac{V_{cs}}{R_3} (R_3 - R_4) + x_2 \cdot R_2 \quad 11$$

$$\dot{x}_1 = \frac{x_4 - x_3}{L_1} + \frac{x_1 (R_3 - R_4 - R_5 - R_1)}{L_2} + \frac{x_2 (R_3 - R_4 - R_5)}{L_1} + \frac{V_{cs} (1 - \frac{R_4}{R_3})}{L_1}$$

We have x_1, x_2, x_3, x_4 from ④, ⑤, ⑥ and ⑦
; Reverse!

$$\begin{bmatrix} V_{L1} \\ V_{L2} \\ i_{L1} \\ i_{L2} \end{bmatrix} = \begin{bmatrix} \frac{R_3 - R_4 - R_5 - R_1}{L_1} & \frac{R_3 - R_4 + R_5}{L_1} & -\frac{1}{L_1} & \frac{1}{L_1} \\ \frac{R_3 + R_4 + R_5}{L_2} & \frac{R_3 + R_4 - R_5 - R_2}{L_2} & 0 & \frac{1}{L_2} \\ \frac{1}{C_1} & 0 & 0 & 0 \\ \frac{1}{C_2} & \frac{1}{C_2} & 0 & 0 \end{bmatrix} \begin{bmatrix} i_{L1} \\ i_{L2} \\ V_{L1} \\ V_{L2} \end{bmatrix}$$

$$+ \begin{bmatrix} \frac{1}{L_1} - \frac{R_1}{L_1 R_3} \\ \frac{1}{L_2} - \frac{R_2}{L_2 R_3} \\ 0 \\ 0 \end{bmatrix} [V_{es}] \quad \begin{aligned} \frac{1}{L_1} \left(\frac{R_4}{R_4 + R_3} \right) \\ L_2 \left(\frac{R_4}{R_4 + R_3} \right) \end{aligned}$$


From ⑤ $V_{R4} = (R_3 - R_4) \left(-x_1 - x_2 - \frac{V_{es}}{R_3} \right)$

$$y = \begin{bmatrix} (R_3 + R_4) & (R_3 - R_4) & 0 & 0 \\ -\frac{R_3 R_4}{R_3 + R_4} & \end{bmatrix} [V_{es}] + \begin{bmatrix} i_{L1} \\ i_{L2} \\ V_{L1} \\ V_{L2} \end{bmatrix} + \begin{bmatrix} 1 + \frac{R_4}{R_3} \end{bmatrix} [V_{es}]$$

$$\frac{R_4}{R_3 + R_4}$$

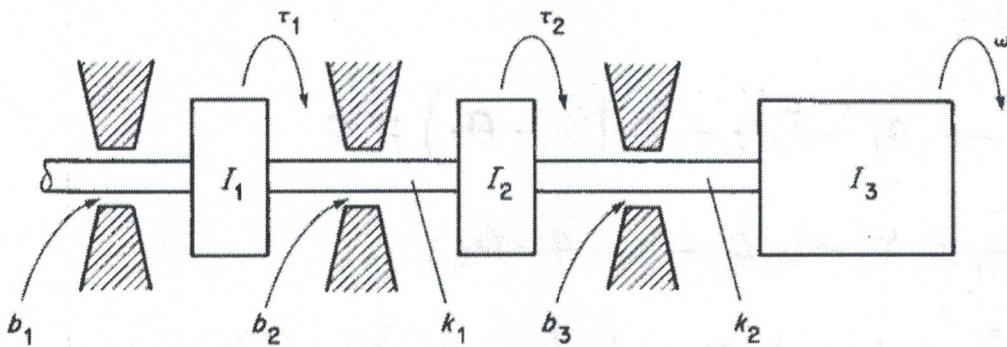Problem 4

(25 %) A two-stage turbine can be modelled, as shown in Fig. 4, by two inertias I_1 and I_2 representing the rotational mass of stage. The stages are coupled by a shaft of stiffness k_1 , and the effective load inertial I_3 is coupled to the turbine by a shaft of stiffness k_2 . The bearing which support the turbine shaft have effective linear frictional coefficients b_1, b_2, b_3 as shown. Assume that the stiffness of the interstage shaft and the turbine load shaft can be split equally either side of the bearing. Write the system dynamical-equation description between the torque inputs stage τ_1, τ_2 ; and the angular velocity of the load ω .



* Inertias I_1, I_2 and I_3 are the loads.

* Shaft stiffness can be modeled as a spring.

* Friction coefficients b_1, b_2, b_3 represents a damping.

* Torques τ_1 and τ_2 are the inputs.

* Newton's Second Law $\rightarrow \ddot{\theta}$ angular acceleration

$$\tau = I \ddot{\theta}$$

State variables


$x_1 = \theta_1$ angular position of I_1

$x_2 = \dot{\theta}_1$ angular velocity of I_1

$x_3 = \theta_2$

$x_4 = \dot{\theta}_2$

$x_5 = \theta_3 ; x_6 = \dot{\theta}_3$

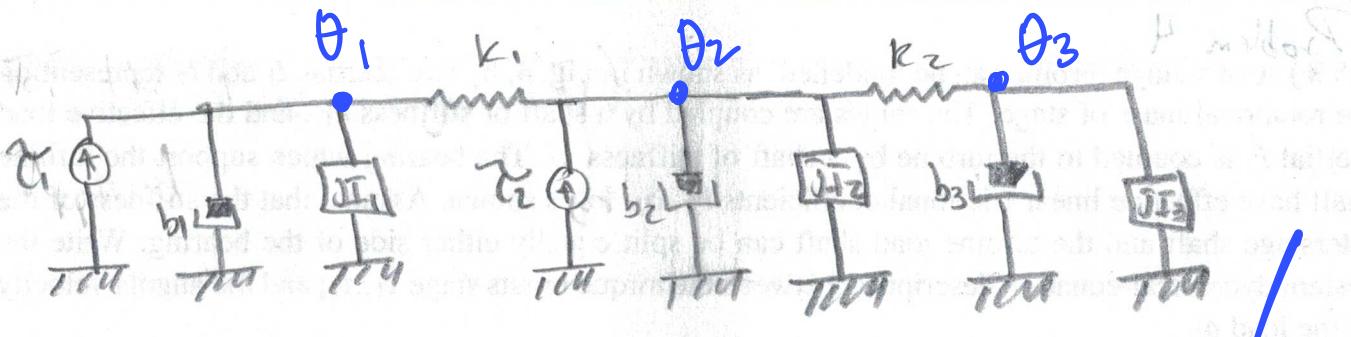

For stage I₁

$$\ddot{x}_1 - b_1 \dot{\theta}_1 - \underbrace{T_1 \ddot{\theta}_1}_{\text{blue bracket}} - k_1 (\theta_1 - \theta_2) = 0$$

$$T_1 \ddot{\theta}_1 = \ddot{x}_1 - b_1 \dot{\theta}_1 - k_1 (\theta_1 - \theta_2)$$

$$\ddot{x}_1 = \frac{\ddot{x}_1}{I_1} - \frac{b_1 \dot{\theta}_1}{I_1} - \frac{k_1 (\theta_1 - \theta_2)}{I_1} \quad (1)$$

For stage I₂

$$\ddot{x}_2 - b_2 \dot{\theta}_2 - \underbrace{T_2 \ddot{\theta}_2}_{\text{blue bracket}} - k_2 (\theta_2 - \theta_1) - k_2 (\theta_2 - \theta_3) = 0$$

$$T_2 \ddot{\theta}_2 = \ddot{x}_2 - b_2 \dot{\theta}_2 - k_2 (\theta_2 - \theta_1) - k_2 (\theta_2 - \theta_3)$$

$$\ddot{x}_4 = \frac{\ddot{x}_2}{I_2} - \frac{b_2 \dot{\theta}_2}{I_2} - \frac{k_2 (\theta_2 - \theta_1)}{I_2} - \frac{k_2 (\theta_2 - \theta_3)}{I_2} \quad (2)$$

Stage I₃

$$T_3 \ddot{\theta}_3 + b_3 \dot{\theta}_3 + k_2 (\theta_3 - \theta_2) = 0$$

$$T_3 \ddot{\theta}_3 = -b_3 \dot{\theta}_3 - k_2 (\theta_3 - \theta_2)$$

$$\ddot{x}_6 = -\frac{b_3 \dot{\theta}_3}{I_3} - \frac{k_2 (\theta_5 - \theta_3)}{I_3} \quad (3)$$

$$\ddot{x}_0 = Ax_0 + Bu ; \dot{x}_1 = x_2 ; \dot{x}_3 = x_4 ; \dot{x}_5 = x_6$$

$$\begin{bmatrix} w_1 \\ x_1 \\ w_2 \\ x_2 \\ w_3 \\ x_3 \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & 0 & 0 & 0 \\ -\frac{k_1}{I_1} & -\frac{b_1}{I_1} & \frac{k_1}{I_1} & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ \frac{k_1}{I_2} & 0 & -\frac{k_1+k_2}{I_2} & -\frac{b_2}{I_2} & \frac{k_2}{I_2} & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & \frac{k_2}{I_3} & 0 & -\frac{k_2}{I_3} & -\frac{b_3}{I_3} \end{bmatrix} \begin{bmatrix} \theta_1 \\ w_1 \\ \theta_2 \\ w_2 \\ \theta_3 \\ w_3 \end{bmatrix}$$

$$+ \begin{bmatrix} 0 & 0 \\ \frac{1}{I_1} & 0 \\ 0 & 0 \\ 0 & \frac{1}{I_2} \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix}$$

✓